

## ANTENNA ANALYZER

**ANTENNA ANALYZER** BY K2ZIA & W8TEE, published in QST magazine, in late 2017.

This new schematic, adds some versatility and also better accuracy to the SWR readings by using a pair of AD8307ARZ Log detectors in place of the original Ge diode version. Some software changes are required for the AD8307 detector. This is available as a modified version of the original Version 110 and can be found in the "SoftwareControlledHamRadio .io" Group in the files area. You need to be a member of this group to access the file.

Alternatively, John Price, WA2FZW, has re-written the software to cater for the AD8307's and the diode detector of the original. Plus many enhancements have been made. As of writing, it's at Version 3.1 and is highly recommended.

The AD8307 detectors used in this version, provide about 25mV per dB in levels from the SWR bridge. When these devices are used, the software must calculate Return Loss, then SWR. As return loss gets lower and lower (ie SWR higher) then for high SWR's calculations over about 8:1, the precision of the calculations is less.

Provision on the PCB is made to add a push button switch (at 'JK3') to allow fine frequency tune, digit selection in some of the Menu items. (Requires WA2FZW software)

A reverse polarity diode is added to provide some protection in case of reversed input voltage supply. This applies more so if the MINI\_360 converter is not used. A suitable Zener could also be used.

Some PCB links have been added, (JK4, JK5) which can be used if the project is to run directly from a 5V supply. i.e. with the MINI\_360 not fitted. Typically a Li\_Po 'battery bank, as used to charge Cell Phones, for example. In this case, the MINI\_360 inverter is not fitted.

**NOTE:-** the Schematic for the vk3pe AA board, does not have the same reference numbers as the original board. I made this PCB for myself only originally, so that was not a consideration. So, when you use Jacks build information, please take this into account.

**ERROR:-** The schematics and PCB for Version '1.2' show R14 and R15 are duplicated. This is not supposed to happen with a PCB package, but somehow it crept through. **The values for R14 & R15 in the SWR bridge area only, should be 4.7 ohms.**

**This will be corrected in the Gerber files and updated to Vers '2.2', dated 260118.** The correct resistors in the SWR area are now R11 and R20, 4.7 ohms.

**ERROR:-** Resistor values for R12, R14 & R16 are now 2k (2000ohms) 2k2 is ok also (2200ohm)  
And for R19, R15 & R17 are now 1k ohm

12<sup>th</sup> Feb, 2018      Vers 1.2 & 2.2 PCB's.  
<VK3PE>

<b>VERSION 2.2 PCB</b>	<b>AA_THROUGH-HOLE VERSION BILL OF MATERIAL</b>			
	240118 DRAFTED by vk3pe			
	<b>250118 CORRECTION</b> , duplicate R14 and R15 on PCB and Schematic !!			
	For the Version 2.2 PCB, they are now R11 & R20.			
	<b>180218</b> R12, R14 & R16 are now 2K. R19, R15 & R17 are now 1k.			
	Read this in conjunction with the build information by Jack, W8TEE.			
	<b>NOTE: the reference numbers are NOT the same as Jacks original PCB.</b>			
Part Type	Designator	Footprint	Description	comments
0R	R4	This part is NOT used.	Resistor	NOT used
100nF	C2	CAP_CER	Capacitor ~5mm pitch	
100nF	C3	CAP_CER	Capacitor ~5mm pitch	
100nF	C14	CAP_CER	Capacitor ~5mm pitch	
100nF	C1	CAP_CER	Capacitor ~5mm pitch	
100nF	C902	CAP_CER	Capacitor ~5mm pitch	
100nF	C6	CAP_CER	Capacitor ~5mm pitch	
100nF	C7	CAP_CER	Capacitor ~5mm pitch	
100nF	C4	CAP_CER	Capacitor ~5mm pitch	
100nF	C5	CAP_CER	Capacitor ~5mm pitch	
100R/1%	R10	AXIAL 0.4" PITCH	Resistor	
100R/1%	R9	AXIAL 0.4" PITCH	Resistor	
100R/1%	R7	AXIAL 0.4" PITCH	Resistor	
100R/1%	R8	AXIAL 0.4" PITCH	Resistor	
100R/1%	R6	AXIAL 0.4" PITCH	Resistor	


100R/1%	R13	AXIAL 0.4" PITCH	Resistor	
10k	R101	AXIAL 0.4" PITCH	Resistor	
10k	R100	AXIAL 0.4" PITCH	Resistor	
150R	R18	AXIAL 0.4" PITCH	Resistor	
150R	R2	AXIAL 0.4" PITCH	Resistor	
1N4001	D2	AXIAL 0.4" PITCH	Diode	
1N4001	D6	AXIAL 0.4" PITCH	Diode	
1N4001	D1	AXIAL 0.4" PITCH	Diode	
1N4001	D5	AXIAL 0.4" PITCH	Diode	
1N4001	D3	AXIAL 0.4" PITCH	Diode	
1nF	C8	CAP_CER	Capacitor ~5mm pitch	
1nF	C9	CAP_CER	Capacitor ~5mm pitch	
2K2	R12	AXIAL 0.4" PITCH	Resistor	
2K2	R14	AXIAL 0.4" PITCH	Resistor	
2K2	R16	AXIAL 0.4" PITCH	Resistor	
39R	R1	AXIAL 0.4" PITCH	Resistor	
1K	R19	AXIAL 0.4" PITCH	Resistor	
1K	R15	AXIAL 0.4" PITCH	Resistor	
1K	R17	AXIAL 0.4" PITCH	Resistor	
47k	R3	AXIAL 0.4" PITCH	Resistor	
50k	RV2	POT_TRIM_3	Trim-Pot	
4.7 ohms	<b>R11</b>	AXIAL 0.4" PITCH	Resistor	
4.7 ohms	<b>R20</b>	AXIAL 0.4" PITCH	Resistor	
AD8307ARZ (SMD)	U2	SOIC-8	Analog Devices chip	
AD8307ARZ (SMD)	U1	SOIC-8	Analog Devices chip	
AD9850_1 (MODULE)	U4	AD9850_2	AD9850 module (ebay)	

Sheet1

HEADER 2	JK2	0.1" pitch header male	0.1" pitch male header single row	the 'unknown Port' connect to BNC socket
HEADER 2	JK3	0.1" pitch header male	0.1" pitch male header single row	locking type preferred
HEADER 2	JK4	0.1" pitch header male	0.1" pitch male header single row	---optional - only required if MINI_360 is not used
HEADER 2	JK5	0.1" pitch header male	0.1" pitch male header single row	---optional - only required if MINI_360 is not used
HEADER 4 right angle	JK1	0.1" pitch header male	0.1" pitch male header single row	NB right angle type !
HEADER 5	JP1	0.1" pitch header male	0.1" pitch male header single row	locking type preferred
LCD_35	LCD1	TFT_3.5	mcufriend TFT display	
MINI_MEGA	U3	MINI_MEGA	Mini Arduino MEGA board	
NOT USED	R5	AXIAL 0.4" PITCH	part not used	NOT used
VR_MINI_360	U5	VR_MINI_360	DC-DC converter module (eBay)	
Dual row headers to suit MEGA board fitting			can use 2 a single row	refer to Jacks build info
Single row header socket to suit AD9850 module			can use 2 a single row	refer to Jacks build info
Single row header socket to mate with JK3, JP1, JK1				see picture of vk3pe board.
Dual row socket to suit AD9850 module			can use 2 a single row	refer to Jacks build info
Rotary encoder with push button switch				refer to Jacks build info
Push Button switch				Optional if using WA2FZW's software
Hardware, nuts. Bolts etc for your mounting method				refer to Jacks build info
Case				refer to Jacks build info
Wire, solder etc				refer to Jacks build info
PCB V2.1 or 2.2 by vk3pe				

# K2ZIA / W8TEE: ANTENNA ANALYZER, WITH MODS FOR AD8307

## VERSION 2.2 THRU HOLE VERSION

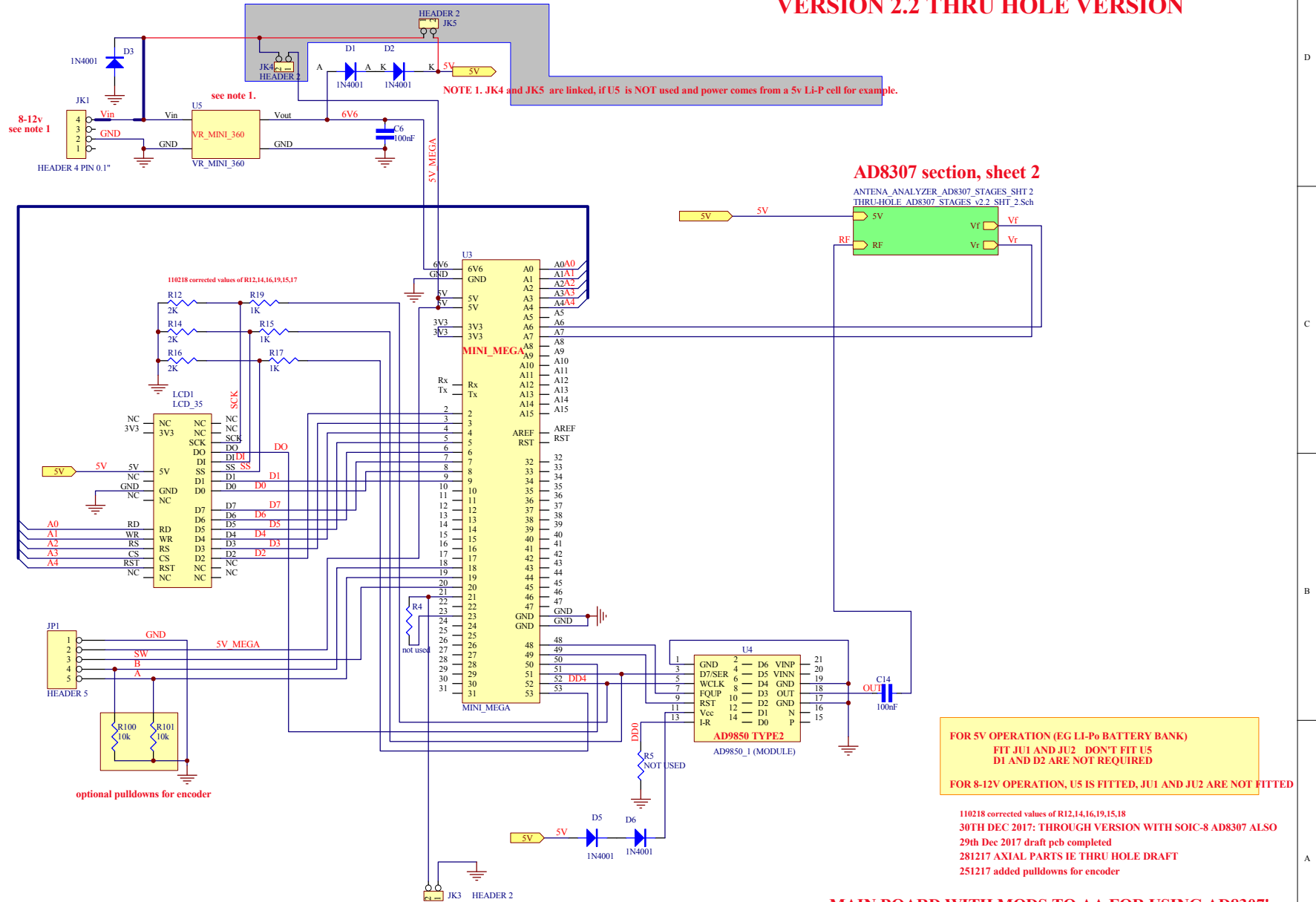

### MAIN BOARD WITH MODS TO AA FOR USING AD8307's

optional push button switch for fine tune (John Price software only)  
Link Arduino 21 and 23 above to invoke.

main\_pcb\_thru\_hole\_V1.2\_271217.pcb

# W8TEE/K2ZIA ANTENNA ANALYZER BRIDGE, NEW PCB WITH AD8307

ADJUST THE ATTENUATOR  
VALUES SO THERE IS ABOUT  
70mV AT THE POINT SHOWN.


### THE OUTPUT OF THE DDS IS TOO HIGH.

Do not exceed about 1.8 - 2V DC out of the AD8307.'s

*NOTE:- There was an error in the V1.2 PCB and schematics. R14 and R15 were duplicated and also appear on the other sheet.*

*The PCB itself shows two R14's & R15's also. The VALUE for R14 and R15 are 4.7 ohms (4R7)*

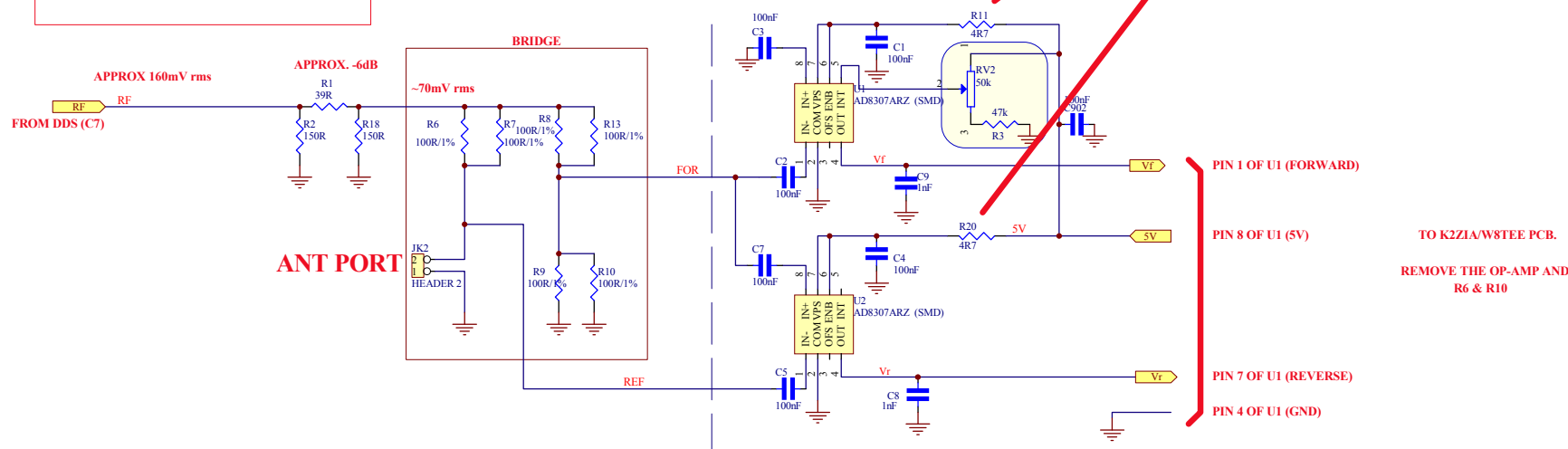*In Version 2.2, this error was corrected and they are now R11 and R20.*



TO ADJUST 'BALANCE'.

WITH NORMAL INPUT SIGNAL AND A SHORT CIRCUIT CONNECTED TO THE PORT, ADJUST THE TRIM-POT SO THAT  $V_f$  AND  $V_r$  ARE EQUAL.

IT'S BEST TO USE A MULTI TURN TRIM POT. FOR RV2

IT'S BEST TO PUT THE METER ACROSS THE  $V_r$  AND  $V_f$  TERMINALS AND ADJUST FOR A ZERO READING.


RV1 IS NOT REQUIRED.

281218 AXIAL PARTS IE THRU HOLE DRAFT  
for pcb version 1a      AA\_MAIN\_AD8307\_2.PCB

03-12-17 6dB pad now.  
01-12-2017 VK3PE


Title		AD8307 BASED BRIDGE FOR THE K2Z1A/W8TEE ANALYZER		DRAWN BY: VK3PE  (C) 2007-2017 and on
Size:	A3	Date: 12-Feb-2018 Time: 11:46:56	Sheet 2 of 2	



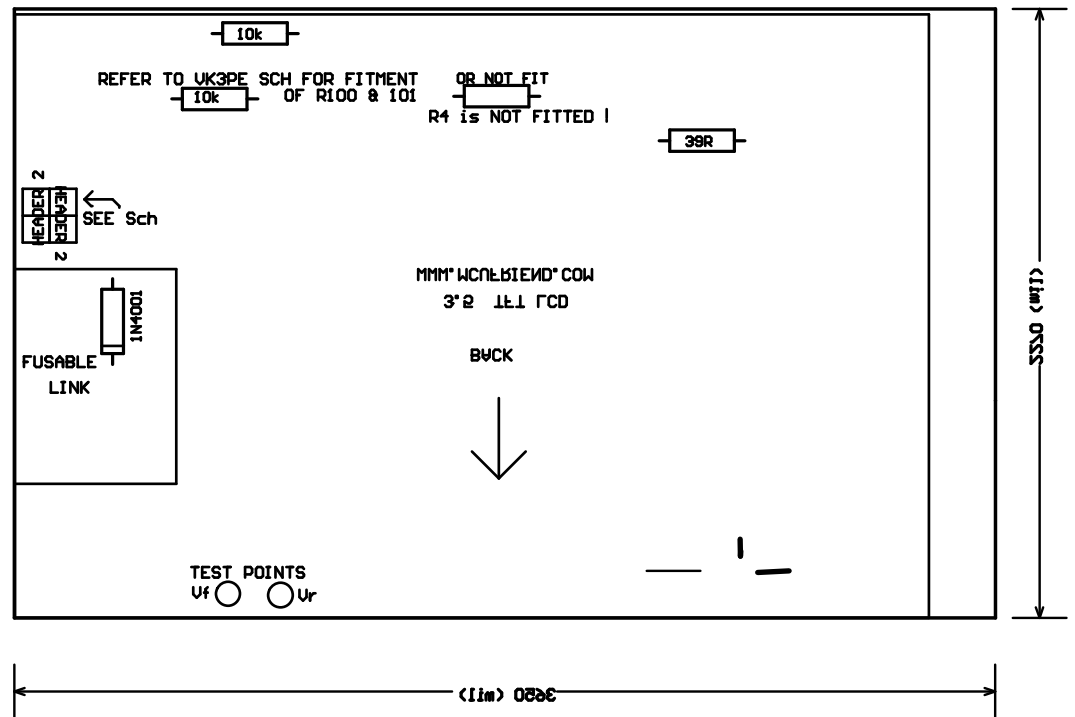





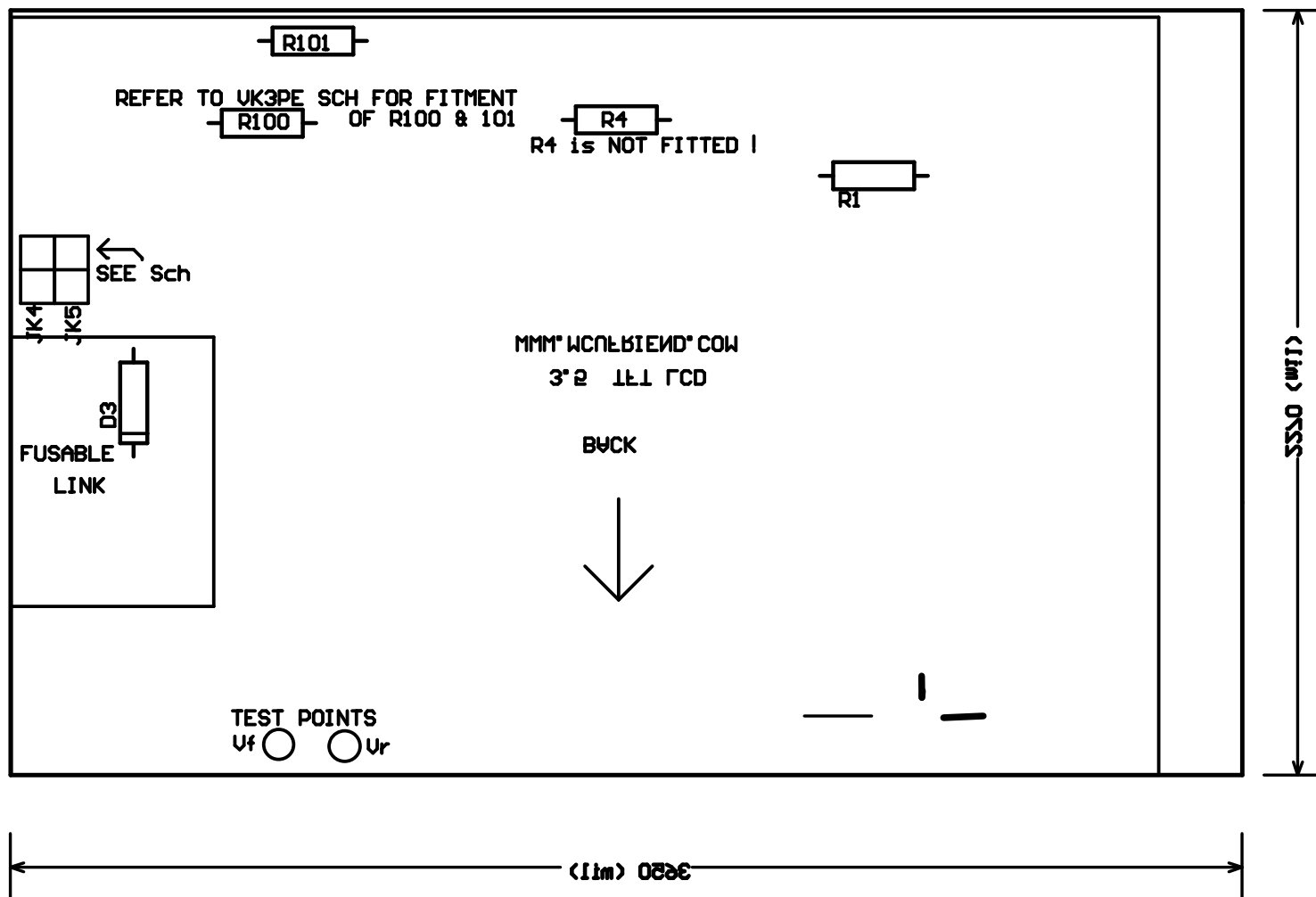


<b>v1.2 PCB</b>	<b>AA_THROUGH-HOLE VERSION BILL OF MATERIAL</b>			
	240118 DRAFTED by vk3pe			
	<b>250118 CORRECTION</b> , duplicate R14 and R15 on PCB and Schematic !!			
	For the Version 2.2 PCB, they are now R11 & R20.			
	<b>180218</b> R12, R14 & R16 are now 2K. R19, R15 & R17 are now 1k.			
	Read this in conjunction with the build information by Jack, W8TEE.			
	<b>NOTE: the reference numbers are NOT the same as Jacks original PCB.</b>			
Part Type	Designator	Footprint	Description	comments
0R	R4	This part is NOT used.	Resistor	NOT used
100nF	C2	CAP_CER	Capacitor ~5mm pitch	
100nF	C3	CAP_CER	Capacitor ~5mm pitch	
100nF	C14	CAP_CER	Capacitor ~5mm pitch	
100nF	C1	CAP_CER	Capacitor ~5mm pitch	
100nF	C902	CAP_CER	Capacitor ~5mm pitch	
100nF	C6	CAP_CER	Capacitor ~5mm pitch	
100nF	C7	CAP_CER	Capacitor ~5mm pitch	
100nF	C4	CAP_CER	Capacitor ~5mm pitch	
100nF	C5	CAP_CER	Capacitor ~5mm pitch	
100R/1%	R10	AXIAL 0.4" PITCH	Resistor	
100R/1%	R9	AXIAL 0.4" PITCH	Resistor	
100R/1%	R7	AXIAL 0.4" PITCH	Resistor	
100R/1%	R8	AXIAL 0.4" PITCH	Resistor	
100R/1%	R6	AXIAL 0.4" PITCH	Resistor	

100R/1%	R13	AXIAL 0.4" PITCH	Resistor	
10k	R101	AXIAL 0.4" PITCH	Resistor	
10k	R100	AXIAL 0.4" PITCH	Resistor	
150R	R18	AXIAL 0.4" PITCH	Resistor	
150R	R2	AXIAL 0.4" PITCH	Resistor	
1N4001	D2	AXIAL 0.4" PITCH	Diode	
1N4001	D6	AXIAL 0.4" PITCH	Diode	
1N4001	D1	AXIAL 0.4" PITCH	Diode	
1N4001	D5	AXIAL 0.4" PITCH	Diode	
1N4001	D3	AXIAL 0.4" PITCH	Diode	
1nF	C8	CAP_CER	Capacitor ~5mm pitch	
1nF	C9	CAP_CER	Capacitor ~5mm pitch	
2K	R12	AXIAL 0.4" PITCH	Resistor	
2K	R14	AXIAL 0.4" PITCH	Resistor	
2K	R16	AXIAL 0.4" PITCH	Resistor	
39R	R1	AXIAL 0.4" PITCH	Resistor	
1K	R19	AXIAL 0.4" PITCH	Resistor	
1K	R15	AXIAL 0.4" PITCH	Resistor	
1K	R17	AXIAL 0.4" PITCH	Resistor	
47k	R3	AXIAL 0.4" PITCH	Resistor	
50k	RV2	POT_TRIM_3	Trim-Pot	
4.7 ohms	<b>R14</b>	<b>NOTE duplicate ref number ! This resistor is in the SWR BRIDGE area</b>		
4.7 ohms	<b>R15</b>	<b>NOTE duplicate ref number ! This resistor is in the SWR BRIDGE area</b>		
AD8307ARZ (SMD)	U2	SOIC-8	Analog Devices chip	
AD8307ARZ (SMD)	U1	SOIC-8	Analog Devices chip	
AD9850_1 (MODULE)	U4	AD9850_2	AD9850 module (ebay)	

Sheet1


HEADER 2	JK2	0.1" pitch header male	0.1" pitch male header single row	the 'unknown Port' connect to BNC socket
HEADER 2	JK3	0.1" pitch header male	0.1" pitch male header single row	locking type preferred
HEADER 2	JK4	0.1" pitch header male	0.1" pitch male header single row	---optional - only required if MINI_360 is not used
HEADER 2	JK5	0.1" pitch header male	0.1" pitch male header single row	---optional - only required if MINI_360 is not used
HEADER 4 right angle	JK1	0.1" pitch header male	0.1" pitch male header single row	NB right angle type !
HEADER 5	JP1	0.1" pitch header male	0.1" pitch male header single row	locking type preferred
LCD_35	LCD1	TFT_3.5	mcufriend TFT display	
MINI_MEGA	U3	MINI_MEGA	Mini Arduino MEGA board	
NOT USED	R5	AXIAL 0.4" PITCH	part not used	NOT used
VR_MINI_360	U5	VR_MINI_360	DC-DC converter module (eBay)	
Dual row headers to suit MEGA board fitting			can use 2 a single row	refer to Jacks build info
Single row header socket to suit AD9850 module			can use 2 a single row	refer to Jacks build info
Single row header socket to mate with JK3, JP1, JK1				see picture of vk3pe board.
Dual row socket to suit AD9850 module			can use 2 a single row	refer to Jacks build info
Rotary encoder with push button switch				refer to Jacks build info
Push Button switch				Optional if using WA2FZW's software
Hardware, nuts. Bolts etc for your mounting method				refer to Jacks build info
Case				refer to Jacks build info
Wire, solder etc				refer to Jacks build info
PCB V2.1 or 2.2 by vk3pe				
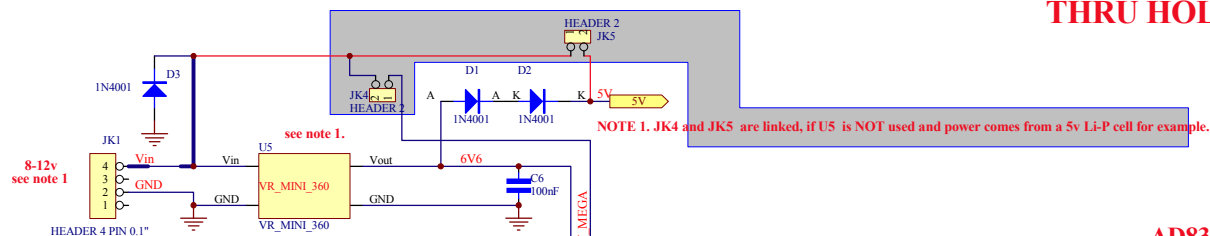
# K2ZIA / W8TEE: ANTENNA ANALYZER, WITH MODS FOR AD8307




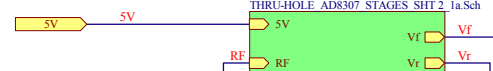**AD8307 section, sheet 2**

ANTENA\_ANALYZER\_AD8307\_STAGES\_SHT 2  
THRU-HOLE AD8307 STAGES SHT 2 1a.Sch



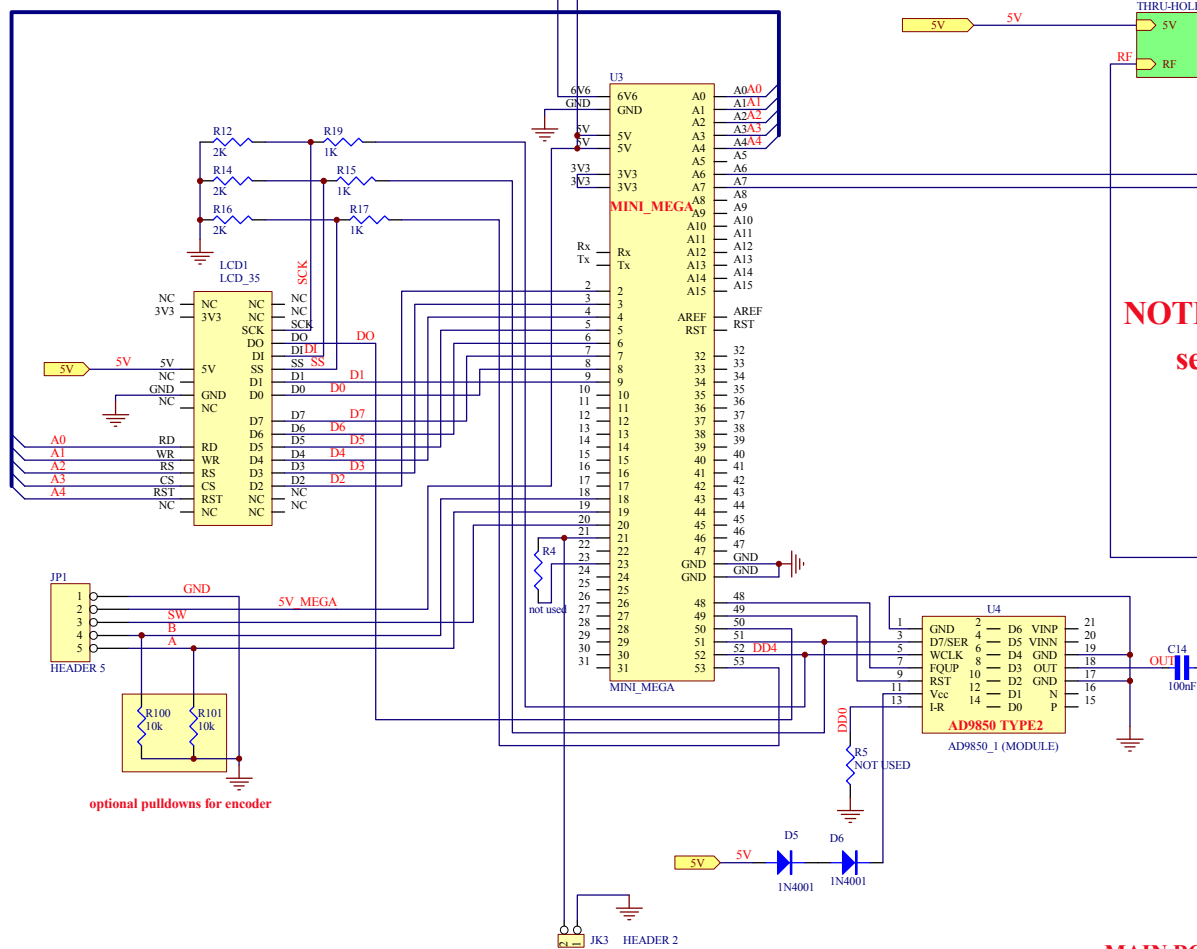**NOTE R14 and R15 are duplicated on the 2nd sheet  
see notes on sheet 2**



**FOR 5V OPERATION (EG LI-PO BATTERY BANK)**  
**FIT JU1 AND JU2 DON'T FIT U5**  
**D1 AND D2 ARE NOT REQUIRED**

**FOR 8-12V OPERATION, U5 IS FITTED, JU1 AND JU2 ARE NOT FITTED**

30TH DEC 2017: THROUGH VERSION WITH SOIC-8 AD8307 ALSO  
29th Dec 2017 draft pcb completed  
281217 AXIAL PARTS IE THRU HOLE DRAFT  
251217 added pulldowns for encoder

## MAIN BOARD WITH MODS TO AA FOR USING AD8307's

**optional push button switch for fine tune (John Price software only)**  
**Link Arduino 21 and 23 above to invoke.**

main pcb thru hole V1.2 271217.pcb

Title <b>THROUGH_HOLE_AA_MAIN</b>			DRAWN BY: <b>VK3PE</b>  (C) 2007-2017 and on
Size: <b>A3</b>	Date: <b>12-Feb-2018</b> Time: <b>11:30:22</b>	Sheet <b>1</b> of <b>2</b>	

# W8TEE/K2ZIA ANTENNA ANALYZER BRIDGE, NEW PCB WITH AD8307

ADJUST THE ATTENUATOR  
VALUES SO THERE IS ABOUT  
70mV AT THE POINT SHOWN.


THE OUTPUT OF THE DDS IS TOO  
HIGH.

Do not exceed about 1.8 - 2V DC out  
of the AD8307's

**NOTE:-** There was an error in the V1.2 PCB and schematics. R14 and R15 were duplicated and also appear on the other sheet.

The PCB itself shows two R14's & R15's also. The VALUE for R14 and R15 are 4.7 ohms (4R7)

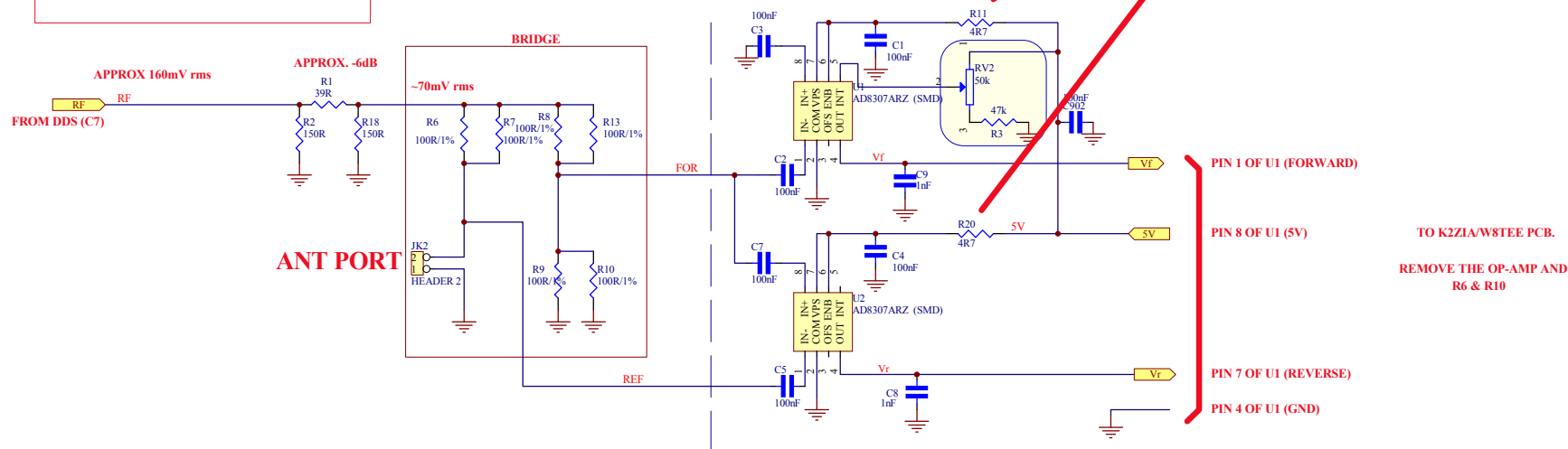In Version 2.2, this error was corrected and they are now R11 and R20.



TO ADJUST 'BALANCE'.

WITH NORMAL INPUT SIGNAL AND A SHORT CIRCUIT  
CONNECTED TO THE PORT, ADJUST THE TRIM-POT  
SO THAT V<sub>f</sub> AND V<sub>r</sub> ARE EQUAL.

IT'S BEST TO USE A MULTI TURN TRIM POT. FOR RV2

IT'S BEST TO PUT THE METER ACROSS THE V<sub>r</sub> AND V<sub>f</sub>  
TERMINALS AND ADJUST FOR A ZERO READING.

RV1 IS NOT REQUIRED.

281218 AXIAL PARTS IE THRU HOLE DRAFT  
for pcb version 1a AA\_MAIN\_AD8307\_2.PCB

03-12-17 6dB pad now.  
01-12-2017 VK3PE  
Title AD8307 BASED BRIDGE FOR  
THE K2ZIA/W8TEE ANALYZER  
Size: A3 Date: 12-Feb-2018 Sheet 2  
Time: 11:33:20 of 2  
DRAWN BY:  
VK3PE  
(C) 2007-2017 and on